



Code No. : 5418/A/N

FACULTY OF ENGINEERING
B.E. 2/4 (Civil) II Sem. (New) (Main) Examination, May/June 2012
ELECTRICAL TECHNOLOGY 'PART - A'

Time: 1½ Hours]

[Max. Marks :38

Note : Answer **all** questions from Part A. Answer **any three** questions from Part B.

PART - A


(14 Marks)

1. State and explain Kirchoff's laws. 4
2. If the length of a wire of resistance 'R' is uniformly stretched to n times its original value, its new resistance is
a) nR b) R/n c) n²R d) R/n² 2
3. Find the following parameters of a voltage $V = 200 \sin 314t$
i) frequency ii) form factor iii) RMS value 3
4. Draw the equivalent circuit diagram of a transformer referred to secondary. 3
5. A single phase induction motor is running at N rpm. Its synchronous speed is N_s. If its slip w.r.t. forward field is
a) S b) - S c) 1 - S and d) 2 - S 2

PART - B

(24 Marks)

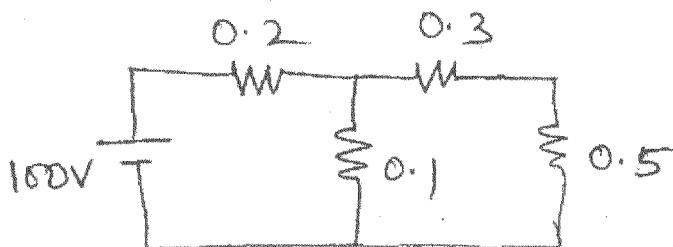
1. a) Derive the equation for voltage and current across a pure inductor 'L' connected to an alternating source. 4
b) Find the equivalent resistance in the circuit given in figure and also find current through it. 4





2. a) Calculate the impedance of the circuit.

3

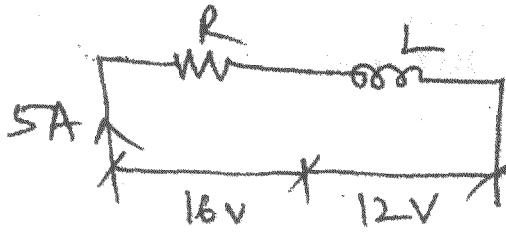

- b) Obtain the relationships between the line and phase values of voltage in a 3- ϕ star-connected system.

5

3. a) With the help of phasor diagram explain no-load transformer.

3

- b) A single-phase, 440/220V, 10 kVA, 50 Hz transformer has a resistance of 0.2Ω and reactance of 0.6Ω on h.v side. The corresponding values of LV side are 0.04Ω and 0.14Ω . Calculate the percentage regulation on full load for 0.8 lagging pf.

5

4. a) Explain principle of operation of induction motor.

4

- b) A 4-pole induction motor has synchronous speed of 1500 rpm at supply frequency 50 Hz. Calculate the slip, if the rated speed is 1440 rpm.

4

5. Write short notes on :

- a) Polar curves

4

- b) Starting of induction motors.

4