



Code No. : 5431/N

FACULTY OF ENGINEERING
B.E. 2/4 (ECE) II Sem. (New) (Main) Examination, May/June 2012
NETWORKS AND TRANSMISSION LINES

Time : 3 Hours]


[Max. Marks : 75

Note : Answer all questions from Part – A. Answer any five questions from Part – B.

PART – A

25 Marks

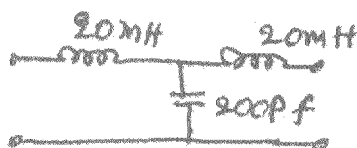1. Define image impedance and iterative impedance. 2
2. Explain need of matching networks in detail. 2
3. What are the advantages of m-derived filters ? How you can choose $m = 0.6$ for terminating half sections ? 3
4. Find cut-off frequency of the filter section. 3




5. What are the applications of equalizers ? 2
6. What are the inverse networks ? Give examples. 3
7. List the properties of positive real function. 2
8. What are the limitations of single stub matching section ? 3
9. What is the condition for distortion less line ? How this is achieved in practice ? 3
10. Show that for a filter $Z_{OT} \times Z_{OTT} = Z_1 Z_2$ 2

PART – B

50 Marks

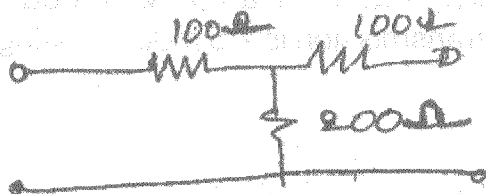11. a) Find the characteristic impedance and attenuation constant of the network show in Fig. below. 5







Code No. : 5431/N

- b) Determine characteristic impedance and propagation constant for given lattice network.

5

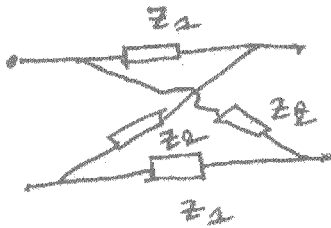

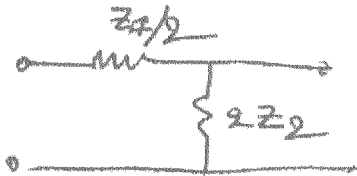12. a) Design L-type matching section to match 500Ω to 400Ω load. 5
 b) Design A composite T-section 'LPF' with following specifications.
 $R_0 = 600 \Omega$, $f_c = 1000 \text{ kHz}$ and $f_{\alpha} = 1200 \text{ kHz}$. 5
13. a) Design a unbalanced asymmetrical π -attenuator with a attenuation of 15 dB to operate between 400Ω and 625Ω line. 5
 b) Derive the expression for $\cosh \gamma$, where γ is image transfer constant for standard symmetrical π -network. 5
14. a) Synthesize $y(s) = \frac{s(s+2)}{(s+1)(s+3)}$. 5
 b) State and explain reactance theorem for LC NW. 5
15. a) Find image impedance z_{i1} and of L-network. 5



- b) Synthesize the function $z(s) = \frac{s^2 + 2s + 6}{s + 3}$. 5
16. a) Define phase velocity and group velocity and establish relation between them in detail. 5
 b) Derive an expression for input impedance of A finite length transmission line. 5
17. a) Explain the properties of Smith Chart. 3
 b) A lossless line with $z_0 = 75 \Omega$ is terminates in an 7 M impedance $Z_R = 115 - j80 \Omega$. The wavelength of the transmission is 2.5 metres. Using the Smith Chart, find :
 a) Standing wave ratio
 b) Max and Min line impedance
 c) Distance between the load and first voltage maximum. 7