



Code No. : 5181/O

FACULTY OF ENGINEERING
B.E. 2/4 (M/P) II Semester (Old) Examination, May/June 2012
BASIC ELECTRONICS

Time : 3 Hours]

[Max. Marks : 75

Note : Answer *all* questions from Part – A. Answer *any five* questions from Part – B.

PART – A

(25 Marks)

1. Differentiate between intrinsic and extrinsic semiconductors. 3
2. Explain the terms : 2
 - i) Mobility
 - ii) Drift current.
3. Why is the FET called a voltage controlled device ? Explain. 3
4. Compare the 3 configurations of the transistor amplifier. 3
5. Draw the circuit for zener diode regulator. 3
6. Write the condition for sustained oscillations of Hartley oscillator. 2
7. What is the advantage of crystal oscillator ? 2
8. Write DeMorgans theorems. 3
9. Draw the symbols for photo diode, LED, SCR and UJT. 2
10. Explain two applications of CRO. 2

PART – B

(50 Marks)

11. a) How is a p-n junction formed ? Draw the circuit diagram of p-n junction diode in forward bias and reverse bias. Explain its operation and give V-I characteristics. 6
b) What is a rectifier ? Draw the circuit diagram for bridge rectifier with LC π filter and explain its operation. 4



12. a) What is a unipolar device ? With neat diagram, explain the operation of JFET and draw its drain and transfer characteristics. 6
- b) What is a regulated power supply ? With neat circuit diagram, explain the operation of zener diode regulator. 4
13. a) List properties of negative feed back amplifiers. State the advantages of negative feed back in amplifiers. Explain the operation of negative feed back amplifier with help of a block diagram. 5
- b) Define oscillator. Derive the condition for getting sustained oscillations in RC phase shift oscillator. 5
14. a) What do you understand by offset voltage and offset current of an OP-Amp ? Explain how an operational amplifier can be used as integrator. 5
- b) Draw and explain the following circuits :
i) Half adder
ii) Full subtractor. 5
15. a) Distinguish between LED and LCD. Explain the construction and operation of UJT. 5
- b) What is LVDT ? Explain the operation of LVDT and give its applications. 5
16. a) What is the difference between TRIAC and DIAC ? With neat diagram, explain the operation of SCR. Give the advantage of TRIAC over SCR. 4
- b) What is the difference between CRT and CRO ? Draw the block diagram of a general purpose CRO and explain function of each block. 6
17. Write short notes on : (5+5)
- a) Hall effect
- b) Strain guage.