

FACULTY OF ENGINEERING

B.E. 2/4 (ECE) I – Semester (New) (Main) Examination, December 2016

Subject: Basic Circuit Analysis


Time: 3 Hours

Max.Marks: 75


Note: Answer all questions from Part A. Answer any five questions from Part B.

PART – A (25 Marks)

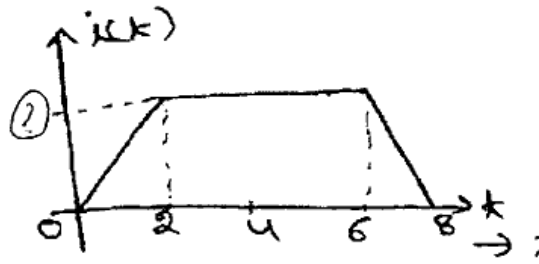
- 1 A current waveform is applied to a 2H inductor. Draw voltage waveform for the given figure. 5



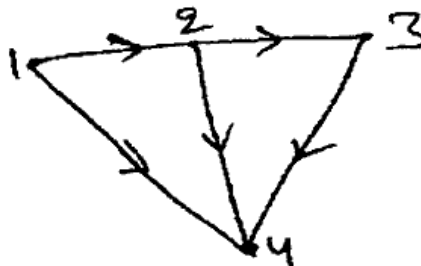- 2 Find Y-parameters of a π -network. 5
3 The given figure shows a graph of the network. Show all the trees of this graph. 4



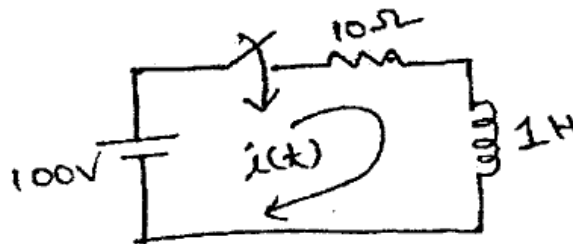- 4 In the given network switch is closed at $t=0$ with zero initial current in the inductor, find $i(t) = \frac{di(t)}{dt}$ at $t=0^+$. 3




- 5 A series circuit consumes 2000 W at 0.5 leading power factor, when connected to 230 V, 50 Hz a.c supply. Calculate: 4
a) Current
b) Apparent power
c) Reactive power
6 A series RLC circuit has the following parameter values $R=10\Omega$, $L=0.01H$, $C=100\mu F$. Compute resonant frequency, bandwidth, lower and upper frequency of the bandwidth. 4

..2


- 10 For the given network a sinusoidal voltage $V = 150 \sin(200t + \phi)$ is applied at $\phi = 30^\circ$ determine current $i(t)$.

10

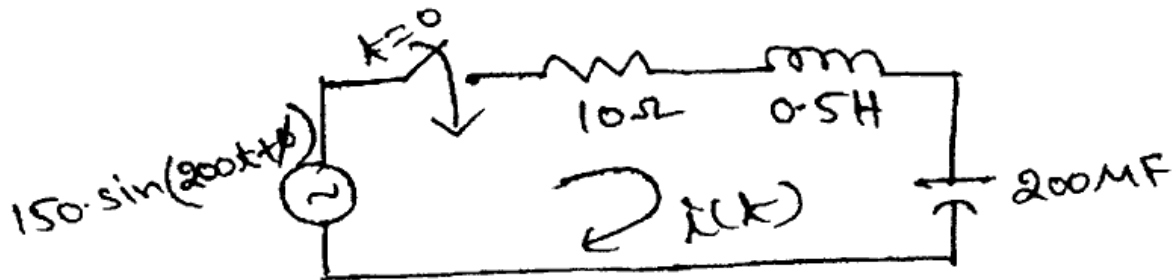

- 11 Find the equivalent T-network for the network shown below,

10

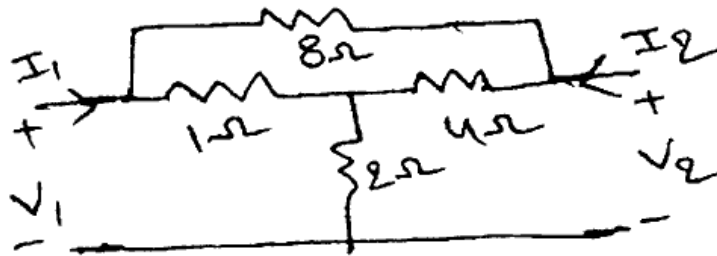

- 12 A coil having a resistance of 20Ω and inductance of $200 \mu H$ is connected in parallel with a variable capacitor. This parallel combination is connected in series with a resistance of 8000Ω . A voltage of $230 V, 10^6 Hz$ is applied across the circuit find
- The value of capacitance at resonance
 - Q factor of the circuit
 - Dynamic impedance of the circuit
 - Total circuit current.

10

- 13 Explain the following:

- Kirchoff's laws
- Magnetically coupled circuits
- Impedance and admittance functions

3

3

4

http://www.osmaniaonline.com

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से