

FACULTY OF ENGINEERING
BE 2/4 (ECE) II Semester (Old) Examination, June -2016.

Sub: Pulse, Digital and Switching Circuits.

Time : 3 Hrs.

Max. Marks : 75

Note : Answer All Questions From Part- A and Any Five Questions from Part-B.
PART – 'A' (25 Marks)

1. Show that a Low Pass RC Circuit can function as an Integrator circuit ? (3)
2. State Clamping Circuit Theorem ? (2)
3. Draw the circuit of compensating attenuator and explain ? (3)
4. Explain how a voltage to frequency converter works with a neat circuit diagram? (3)
5. State and prove DeMorgan's Theorem ? (2)
6. Define Prime Implicants & essential prime Implicants ? (2)
7. Realize Half Subtractor using NAND gates ? (2)
8. Draw the logic diagram & Truth table of SR, JK and T Flip Flops ? (3)
9. Convert 'D' Flip Flop to 'T' Flip Flop ? (3)
10. Distinguish between state table and Excitation table ? (2)

PART – B (50 Marks)

11. a) Why a High Pass RC circuit is called a differentiator ? (3)
b) 1 KHz symmetrical square wave of ± 10 v is applied to Low Pass RC circuit having 1 ms time constant. Calculate and plot the output ? (7)
12. a) Design collector coupled mono stable multi vibrator using a NPN transistor. Neglect I_{CBO} and the Junction voltages. Assume $h_{FE(min)}=20$, $V_{BE}=-1V$ for the transistor in cut-off and $I_B=1.5 I_{B(min)}$ for the transistor in saturation, $V_{CC}=8V$, $I_{C(sat)}=2mA$, $T=2ms$, and $R_1=R_2$, find R_C, R, V_{BB}, R_1 and C ? (10)
13. a) Design a full adder circuit ? Implement it using 3 to 8 decoder circuit ? (5)
b) Minimize the following function by K-Map Method : (5)
 $f(a,b,c,d,e) = \sum_m (1,2,3,8,9,10,15,16,17,18,22,26,27) + \sum \phi(0,4,11,19,28,30,31)$? <http://www.osmaniaonline.com>
14. a) Explain hazards in Digital Circuit with examples ? (4)
b) Design a Code Converter which converts BCD to Excess-3 code ? (6)
15. Design a Mod-8 Synchronous counter using JK flipflops. (10)
16. a) Differentiate between Synchronous & Asynchronous sequential circuits. (5)
b) Design a 3-bit Asynchronous Ripple counter using JK flipflop. (5)
17. Write a short notes on any TWO : (5+5)
 - a) QuineMcClusky tabulation method.
 - b) Switching hazards.
 - c) Negative peak clamper circuit.
 - d) UJT.
