

**FACULTY OF ENGINEERING****B.E VI Semester (CBCS)(EEE) (Main) Examination, May / June -2019****Subject: Basics of Power Electronics (Elective –I)****Time: 3 hours****Max. Marks: 70****Note: Answer all questions from Part – A, & answer any five questions from Part – B****PART – A (20 Marks)**

- 1 List the advantages of power electronic converters. 2
- 2 What is meant by commutation? List the methods for commutating SCR. 2
- 3 Explain how a freewheeling diode improves power factor in a system. 2
- 4 What is a dual converter? List the advantages of a dual converter. 2
- 5 Enumerate the applications of D.C choppers. 2
- 6 A step up chopper has output voltage of two to four times the input voltage. For a chopping frequency of 2000Hz, determine the range of off periods for the gate signal. 2
- 7 What is an inverter? List few industrial applications of inverter. 2
- 8 List the pulse width modulation techniques used for inverter control. 2
- 9 A single phase full wave ac voltage controller feeds a load of  $R=20\Omega$  with an input voltage of 230V, 50Hz. Find the rms value of output voltage if firing angle is  $45^\circ$ . 2
- 10 List the advantages of circulating mode of operation in cycloconverter. 2

**PART – B (50 Marks)**

- 11 a) Explain the switching performance of BJT with relevant waveforms. Indicate clearly turn-on and turn-off times and their components. 5+5
- b) Draw and explain the switching characteristics of a thyristor.
- 12 Describe the operation of a single phase two-pulse converter with relevant voltage and current waveforms and obtain an expression for the output voltage. 10
- 13 Describe the working of buck-boost converter with neat wave forms. Derive the expression for output voltage. 10
- 14 Discuss the working principle of a three phase inverter with neat waveforms for a star connected resistive load, when each thyristor operates for  $180^\circ$  mode. 10
- 15 Discuss the principle of phase control in single phase ac voltage controller. Derive expression for the rms value of its output voltage. 10
- 16 a) Explain with relevant circuit diagram and waveforms how complementary impulse commutation is achieved?
- b) A 3- $\Phi$  full converter charges a battery from a three phase supply of 230V, 50Hz. The battery emf is 200V and its internal resistance is  $0.5\Omega$ . On account of inductance connected in series with the battery, charging current is constant at 20A. Compute the firing delay and the supply power factor. 5+5
- 17 Explain any two from the following
  - a) Thyristor Protection
  - b) Sinusoidal pulse width modulation
  - c) Step up cyclo converter
 5+5

\*\*\*\*\*